

## ADDER

---

### 2.1 PURPOSE

This lab builds a full 1-bit adder, but the intent is to continue to familiarize students with *Logisim-Evolution* and how basic arithmetic functions can be completed using simple gate-level logic. Additionally, this lab develops an automated testing system that will be used to test future lab submissions.

### 2.2 PROCEDURE

#### 2.2.1 Half-Adder

Open Logisim and start a new project. In *Logisim-Evolution* circuits can contain any number of sub-circuits. Subcircuits fill the same role in a physical circuit as a function or procedure fills in a software project. A new subcircuit can be added to a circuit by clicking PROJECT -> ADD CIRCUIT. Name the new circuit **Half\_Adder**. Open the new subcircuit by double-clicking its name in the Explorer Pane.

Because this is a new subcircuit, the drawing canvas is blank. A half-adder is a circuit that will add two input bits. Because it is possible to add two bits and generate a carry, the half-adder must allow for a carry out bit. Figure 2.1 is the circuit diagram for a half-adder.

 


Figure 2.1: Half-Adder

This is fairly easy to build. Component U1 is an XOR gate and U2 is an AND gate. There are two inputs and two outputs and all of the devices should be connected as shown. To test the circuit, whenever input A and input B are different the Sum should be high and when input A and input B are both high the CO (Carry Out) bit should also be high.

### 2.2.2 Full Adder

A full adder takes two input bits and adds them, like a half-adder, but it also includes the logic necessary to input or output a carry bit so it can be cascaded with other adders. Figure 2.2 is the logic diagram for a full adder.

 


Figure 2.2: Full Adder

Create a new subcircuit named **Full\_Adder** and wire all of the components as illustrated in Figure 2.2. Notice that U1 and U2 are XOR gates, U3 and U5 are AND gates, and U4 is an OR gate. There are also three inputs and two outputs.

### 2.2.3 Main Circuit

In most *Logisim-Evolution* projects, the **main** circuit is used to provide a nice user interface for the project. Typically, various subcircuits are dropped onto the main circuit canvas and various inputs and outputs are wired to them. A user can then test the project without worrying about the details of the subcircuits.

For this project, open the **main** circuit by double-clicking its name in the Library panel. Click one time on the **Full\_Adder** subcircuit then move the mouse over the drawing canvas. Notice that the mouse pointer has changed into a representation of the subcircuit. Drop that subcircuit anywhere on the drawing canvas and then wire the various inputs and outputs as shown in Figure 2.3.

 


Figure 2.3: Full Adder

This circuit can be tested by using the *poke* tool and entering these values. After each line, check to see that the outputs are correct.

Inputs			Outputs	
A	B	CI	Sum	CO
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

Table 2.1: Test Vector For Full Adder

#### 2.2.4 Automated Testing

While it is possible to use the *poke* tool and check the outputs for various input combinations, as digital logic circuits become more complex it is important to automate the testing process so no input combinations are overlooked. *Logisim-Evolution* includes a **SIMULATE -> TEST VECTOR** feature that is used for automating circuit testing.

The first step in using automatic testing is to create a *Test Vector* file. This is a simple *.txt* file that can be created in any text processor, like *Notepad*. The format for a test vector is fairly simple.

- Every line is a single test of the circuit, except the first line.
- The first line defines the various inputs and outputs being tested.
- Any line that starts with a hash mark (#) is a comment and is ignored.

*Do not use a word processor to create the Test Vector since that would add unneeded codes for things like fonts and margins.*

Following is the test vector file used to test the `main` circuit.

---

```

1  # Test vector for Adder
2  CI A B Sum CO
3  0 0 0 0 0
4  0 0 1 1 0
5  0 1 0 1 0
6  0 1 1 0 1
7  1 0 0 1 0
8  1 0 1 0 1
9  1 1 0 0 1
10 1 1 1 1 1

```

---

Following is an explanation for the *Test vector for Adder* file.

LINE 1 This is just the title of the file. Because this line starts with a hash (#) it is a comment and will be ignored by *Logisim-Evolution*.

LINE 2 This line lists all of the inputs and outputs in the circuit under test. In this case, there are three inputs, *CI*, *A*, and *B*, along with two outputs, *Sum* and *CO*. *Logisim-Evolution* is able to determine whether the pin is an input or output from its properties.

LINE 3 This line contains the first test for the circuit. This line specifies that *Logisim-Evolution* make *CI*, *A*, and *B* equal to zero and then check to be certain that *Sum* and *CO* are also zero.

OTHER LINES All other lines set the three input bits and specify the expected response in the output bits.

To start a test, click SIMULATE -> TEST VECTOR. The window illustrated in Figure 2.4 opens.

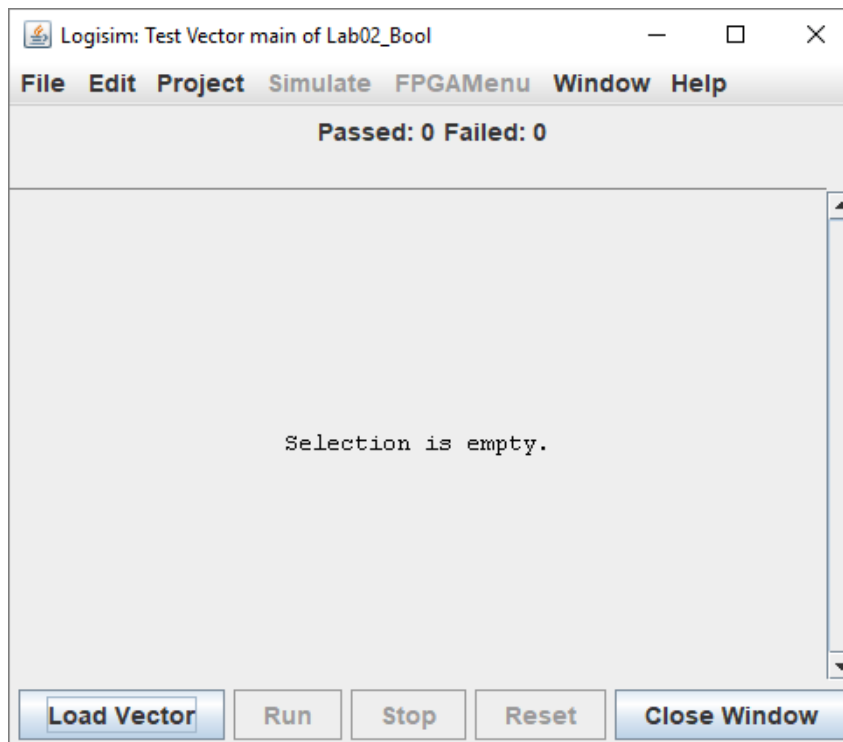


Figure 2.4: Test Vector Window

Click the *Load Vector* button at the bottom of the window and load the test vector file. The test will automatically start and *Logisim-Evolution* will report the results, like in Figure 2.5.

 


Figure 2.5: Test Completed

The test indicates all 8 lines passed and zero failed so it could be reasonably concluded that the circuit is functioning properly. Figure 2.6 illustrates a failed test. The circuit designer would then need to troubleshoot to determine what went wrong with the circuit.

*An error was intentionally added to the test vector file to generate a failed test.*

status	CI	A	B	Sum	CO
fail	1	1	1	1	1
pass	0	0	0	0	0
pass	0	0	1	1	0
pass	0	1	0	1	0
pass	0	1	1	0	1
pass	1	0	0	1	0
pass	1	0	1	0	1
pass	1	1	0	0	1

Figure 2.6: Test Failure

*Note: the test vector files for all labs are made available to students so they can check their work prior to submitting them.*

## 2.3 DELIVERABLE

To receive a grade for this lab, build both the half-adder and full adder and then add the full adder to the **main**. It is important to ensure the input and output pin names are the same as in the lab instructions since a test vector will be used to check the circuit. Be sure the standard identifying information is at the top left of the **main** circuit, similar to:

George Self  
 Lab 02: Adder  
 September 17, 2019

Save the file with this name: *Lab02\_Adder* and submit that file for grading.